



**Q1/**Design a full adder using two half adders and one OR Gate. (10 marks)

**Q2/**Design 4 bit PISO. (10 marks)

**Q3/** Design a combinational circuit whose input is a 3-bit number and whose output is the 2's complement of the input number. (10 marks)

**Q4/**Answer **ONE** branch only (10 marks)

- A. Design 8 to 1 Multiplexer from 4 to 1 multiplexes and 2 to 1 Multiplexer.
- B. Design 1 to 4 Demultiplexer and show the truth table and equation & combinational circuit.

**Q5/** A combinational circuit is defined by the following three Boolean functions

(10 marks)

$$F_1(A, B, C) = \sum m(0,3,4)$$

$$F_2(A, B, C) = \sum m(1,2,7)$$

$$F_3(A, B, C) = \prod M(0,1,2,4)$$

Implement the circuit with a decoder and external OR gates.

**Q6/**

A- Simplifying **THREE** of the following Boolean function using k-map (12 marks)

1.  $F(W, X, Y, Z) = \sum m(0,1,2,4,5,6,8,9,12,13,14)$

2.  $F = \bar{A}\bar{B}\bar{C} + \bar{B}C\bar{D} + A\bar{B}\bar{C} + \bar{A}BC\bar{D}$

3.  $F = (\bar{A} + \bar{C}).(A + B + D).(A + \bar{B} + C).(\bar{A} + \bar{B} + \bar{D})$

4.  $F(W, X, Y, Z) = \sum m(4,6,7,8,12,15), d(W, X, Y, Z) = \sum m(2,3,5,10,11,14)$

B- Simplify the Boolean Function F and implemented it with NAND and NOR gates

(8 mark)

$$F = A\bar{C} + ACE + AC\bar{E} + \bar{A}C\bar{D} + \bar{A}\bar{D}\bar{E}$$