

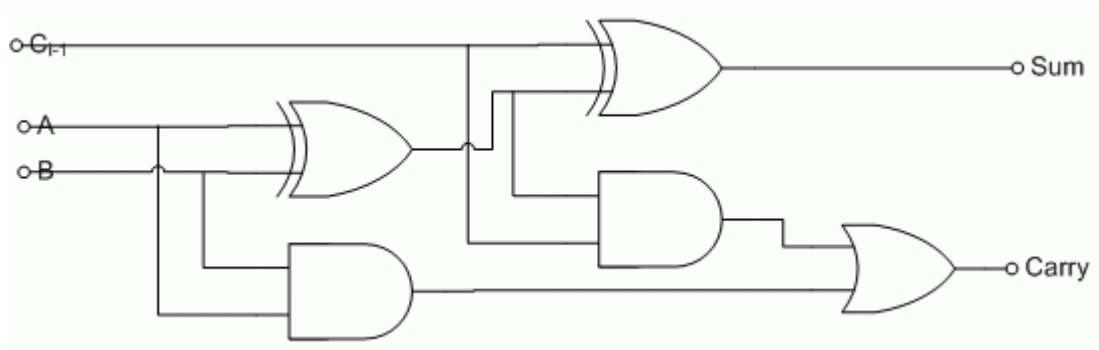


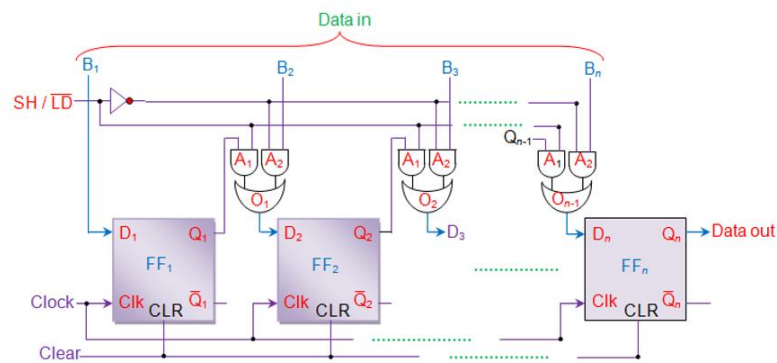Q1/Design a full adder using two half adders and one OR Gate.




Q2/Design 4 bit PISO.

Drawing any one of follow is correct

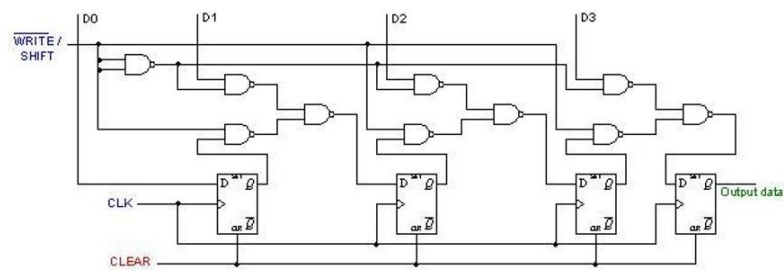



2016 - 2017

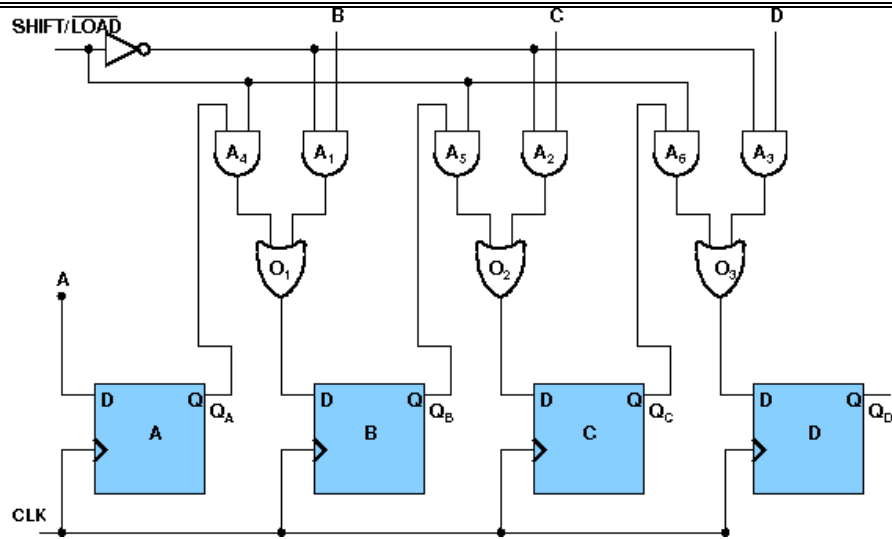

Q3/ Design a combinational circuit whose input is a 3-bit number and whose output is the 2's complement of the input number.

| QA ₁ | A ₂ | A ₃ | | F ₁ | F ₂ | F ₃ | F ₄ |
|-----------------|----------------|----------------|--|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | | 0 | 0 | 0 | 1 |

F₁

| | | | |
|---|--|--|--|
| 1 | | | |
| | | | |

$$F_1 = \overline{A_1} \overline{A_2} \overline{A_3}$$

F₂

| | | | |
|---|---|---|---|
| | 1 | 1 | 1 |
| 1 | | | |

$$F_2 = A_1 \overline{A_2} \overline{A_3} + \overline{A_1} A_3 + \overline{A_1} A_2$$



2016 - 2017

F₃

| | | | |
|--|---|--|---|
| | 1 | | 1 |
| | 1 | | 1 |


$$F_3 = \bar{A}_2 A_3 + A_2 \bar{A}_3$$

$$F_3 = A_2 \oplus A_3$$

F₄

| | | |
|--|---|---|
| | 1 | 1 |
| | 1 | 1 |

$$F_4 = A_3$$

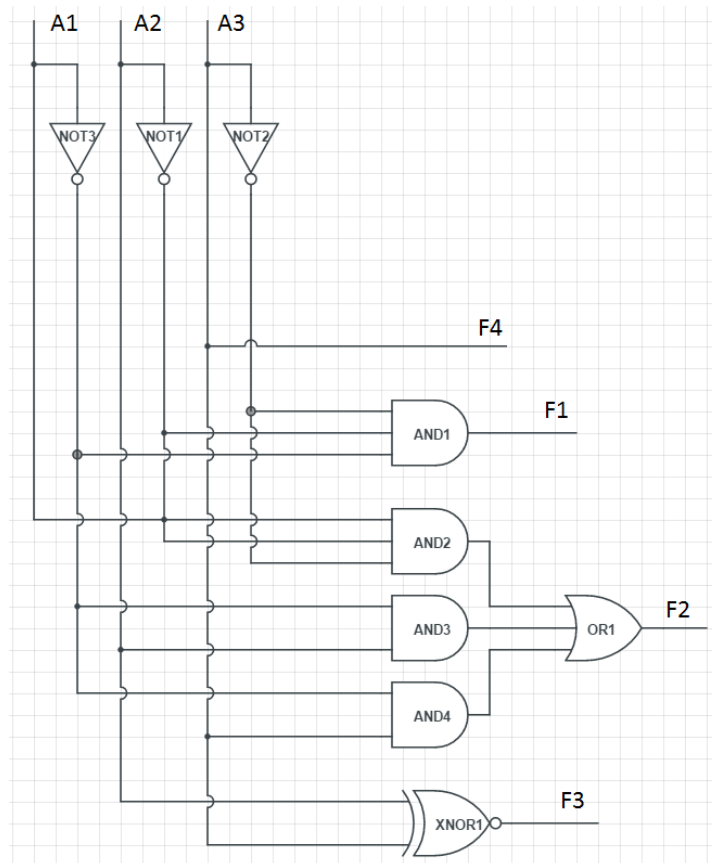


Q4/Answer ONE branch only

A. Design 8 to 1 Multiplexer from 4 to 1 multiplexes and 2 to 1 Multiplexer.



2016 - 2017

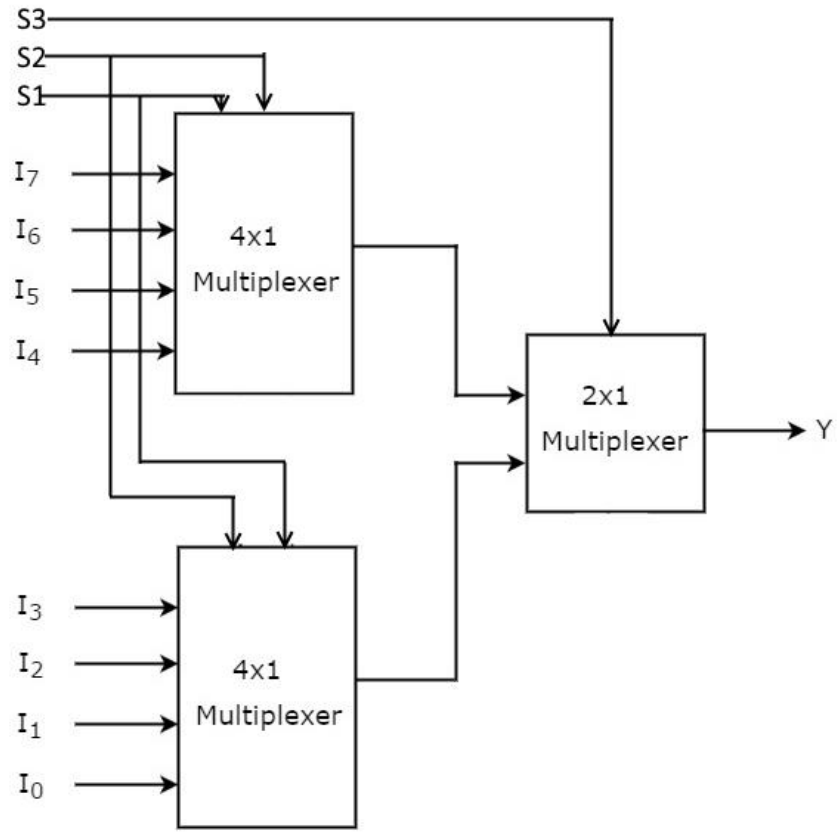

Q5/ A combinational circuit is defined by the following three Boolean functions

$$F_1(A, B, C) = \sum m(0,3,4)$$


$$F_2(A, B, C) = \sum m(1,2,7)$$

$$F_3(A, B, C) = \prod M(0,1,2,4)$$

Implement the circuit with a decoder and external OR gates.



2016 - 2017

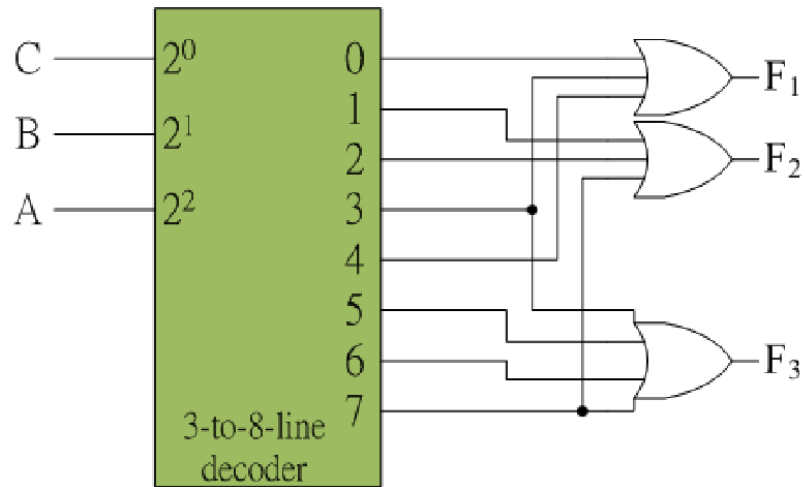

Q6/

1. $F(W, X, Y, Z) = \sum m(0,1,2,4,5,6,8,9,12,13,14)$

| | | |
|---|---|---|
| 1 | 1 | 1 |
| 1 | 1 | 1 |
| 1 | 1 | 1 |
| 1 | 1 | |

$F(w, x, y, z) = \bar{y} + \bar{w}z + xz$

2. $F = \bar{A}\bar{B}\bar{C} + \bar{B}C\bar{D} + A\bar{B}\bar{C} + \bar{A}BC\bar{D}$

| | | |
|---|---|---|
| 1 | 1 | 1 |
| | | 1 |
| | | |
| 1 | 1 | 1 |

$F = \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}C\bar{D}$



2016 - 2017

3. $F(W, X, Y, Z) = \sum m(4,6,7,8,12,15), d(W, X, Y, Z) = \sum m(2,3,5,10,11,14)$

| | | | |
|---|---|---|---|
| | | x | x |
| 1 | x | 1 | 1 |
| 1 | | 1 | x |
| 1 | | x | x |

$$F(w, x, y, z) = y + x\bar{z} + w\bar{z}$$

$$F(w, x, y, z) = y + \bar{w}x + w\bar{z}$$

B- Simplify the Boolean Function F and implemented it with NAND and NOR gates

$$F = A\bar{C} + ACE + ACE\bar{E} + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{D}\bar{E}$$